

1 Test Section

2083 Baishakh — Question 1

Find the current in 10 V source using nodal analysis.

